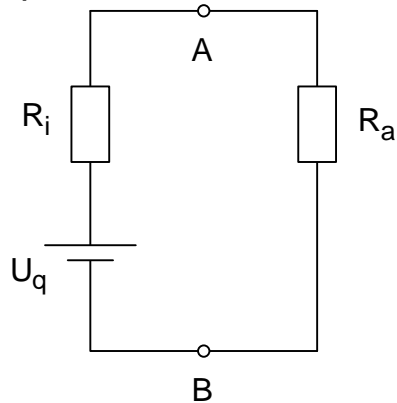


NEISSE - ELEKTRO 2000

LÖSUNGEN


1

a)



b)
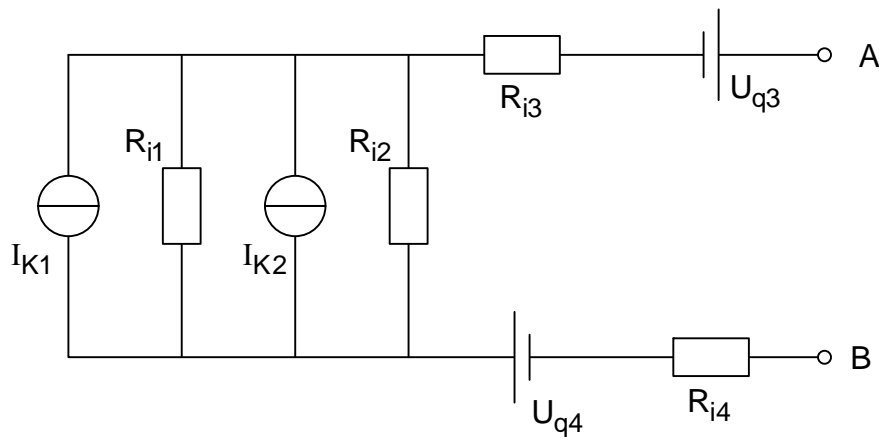
$$R_a = \left[\left((R_4 \parallel R_5 \parallel R_6) + (R_2 \parallel R_3) \right) \parallel R_7 \right] + R_1 = \underline{\underline{14,545 \Omega}}$$




$$I_{K1} = \frac{U_{q1}}{R_{i1}} = 2 \text{ A}$$

$$I_{K2} = \frac{U_{q2}}{R_{i2}} = 2 \text{ A}$$

$$I_{K12} = I_{K1} + I_{K2} = 4 \text{ A}$$

$$R_{i12} = \frac{R_{i1} R_{i2}}{R_{i1} + R_{i2}} = 0,5 \Omega$$
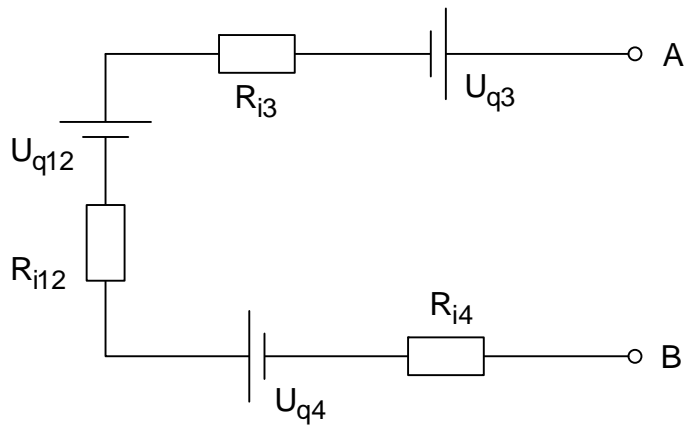
$$\Rightarrow U_{q12} = I_{K12} \cdot R_{i12} = 2 \text{ V}$$



$$U_q = U_{q1} + U_{q2} + U_{q3} = 6 \text{ V}$$

$$R_i = R_{i12} + R_{i3} + R_{i4} = 2,5 \Omega$$

	$R_i = 2,5 \Omega$ $R_a = 14,545 \Omega$ $U_q = 6 \text{ V}$ $U_{AB} = I \cdot R_a = 0,352 \text{ A} \cdot 14,545 \Omega$ $= 5,12 \text{ V}$
--	--

c)

$$I = I_1 = \frac{U_q}{R_a + R_i} = \frac{6 \text{ V}}{17,045 \Omega} = \underline{\underline{0,352 \text{ A}}} \Rightarrow U_1 = 3,52 \text{ V}$$

$$\frac{I_7}{I_1} = \frac{(R_2 \parallel R_3) + (R_4 \parallel R_5 \parallel R_6)}{R_7 + (R_2 \parallel R_3) + (R_4 \parallel R_5 \parallel R_6)}$$

$$I_7 = 0,4545 I_1 = 0,4545 \cdot 0,352 \text{ A}$$

$$= \underline{\underline{0,16 \text{ A}}} \Rightarrow U_7 = 1,6 \text{ V}$$

Knotensatz: $-I_1 + I_7 + I_{2-6} = 0$

$$I_{2-6} = I_1 - I_7 = 0,192 \text{ A}$$

$$I_2 = I_3 = 0,5 \cdot I_{2-6} = \underline{\underline{0,096 \text{ A}}} \Rightarrow U_2 = U_3 = 0,96 \text{ V}$$

$$I_4 = I_5 = I_6 = 0,33 \cdot I_{2-6} = 0,064 \text{ A} \Rightarrow U_4 = U_5 = U_6$$

$R_a = 14,545 \Omega$	$I_1 = 0,352 \text{ A}$	$U_1 = 3,52 \text{ V}$
$R_i = 2,5 \Omega$	$I_2 = 0,096 \text{ A}$	$U_2 = 0,96 \text{ V}$
$U_q = 6 \text{ V}$	$I_3 = 0,096 \text{ A}$	$U_3 = 0,96 \text{ V}$
$U_{AB} = 5,12 \text{ V}$	$I_4 = 0,064 \text{ A}$	$U_4 = 0,64 \text{ V}$
$I = 0,352 \text{ A}$	$I_5 = 0,064 \text{ A}$	$U_5 = 0,64 \text{ V}$
	$I_6 = 0,064 \text{ A}$	$U_6 = 0,64 \text{ V}$
	$I_7 = 0,16 \text{ A}$	$U_7 = 1,6 \text{ V}$

2

Figure 2a) series connection

a)

$$I = \text{konst.} = 100 \text{ A} \quad S = \text{konst.} \quad S = \frac{I}{A_{\perp}}$$

$$R = \frac{L}{\chi \cdot A} \quad A_{\perp} = 40 \text{ mm}^2$$

$$R = \frac{L}{\chi \cdot A} \left\{ \begin{array}{l} R_1 = \frac{L_1}{\chi_1 \cdot A} = 5 \Omega \\ R_2 = \frac{L_2}{\chi_2 \cdot A} = 2,5 \Omega \\ R_3 = \frac{L_3}{\chi_3 \cdot A} = 1,25 \Omega \end{array} \right.$$

$$U = I \cdot R \left\{ \begin{array}{l} U_1 = I \cdot R_1 = 100 \text{ A} \cdot 5 \Omega = 500 \text{ V} \\ U_2 = I \cdot R_2 = 100 \text{ A} \cdot 2,5 \Omega = 250 \text{ V} \\ U_3 = I \cdot R_3 = 100 \text{ A} \cdot 1,25 \Omega = 125 \text{ V} \end{array} \right.$$

b)

$$E = \frac{U}{d} \left\{ \begin{array}{l} E_1 = \frac{U_1}{d_1} = \frac{500 \text{ V}}{20 \text{ mm}} = 250 \frac{\text{V}}{\text{cm}} = 25 \frac{\text{V}}{\text{mm}} \\ E_2 = \frac{U_2}{d_2} = \frac{250 \text{ V}}{20 \text{ mm}} = 125 \frac{\text{V}}{\text{cm}} = 12,5 \frac{\text{V}}{\text{mm}} \\ E_3 = \frac{U_3}{d_3} = \frac{125 \text{ V}}{20 \text{ mm}} = 62,5 \frac{\text{V}}{\text{cm}} = 6,25 \frac{\text{V}}{\text{mm}} \end{array} \right.$$

Alternativ

$$S = \frac{I}{A} = 2,5 \frac{A}{\text{mm}^2} \quad \left\{ \begin{array}{l} E_1 = \frac{S}{\chi_1} = 25 \frac{V}{\text{mm}} \\ E_2 = \frac{S}{\chi_2} = 12,5 \frac{V}{\text{mm}} \\ E_3 = \frac{S}{\chi_3} = 6,25 \frac{V}{\text{mm}} \end{array} \right.$$
$$E = \frac{S}{\chi}$$

Figure 2b) parallel connection

c)

U = constant

$$U = I \cdot R = \frac{I}{G}$$

$$G = G_1 + G_2 + G_3$$

$$G = \frac{\chi \cdot A}{L} \quad \left\{ \begin{array}{l} G_1 = \frac{\chi_1 \cdot A_1}{L_1} = 0,05 \text{ S} \\ G_2 = \frac{\chi_2 \cdot A_2}{L_2} = 0,1 \text{ S} \\ G_3 = \frac{\chi_3 \cdot A_3}{L_3} = 0,2 \text{ S} \end{array} \right.$$
$$A_1 = A_2 = A_3 = 20 \text{ mm}^2$$
$$L_1 = L_2 = L_3 = 40 \text{ mm}$$

$$G = 0,35 \text{ S}$$

$$U = \frac{I}{G} = 285,71 \text{ V}$$

$$I = U \cdot G \quad \left\{ \begin{array}{l} I_1 = U \cdot G_1 = 14,285 \text{ A} \\ I_2 = U \cdot G_2 = 28,57 \text{ A} \\ I_3 = U \cdot G_3 = 57,143 \text{ A} \end{array} \right.$$

d)

$$S = \frac{I}{A} \quad \left\{ \begin{array}{l} S_1 = \frac{I_1}{A} = 0,714 \frac{A}{\text{mm}^2} \\ S_2 = \frac{I_2}{A} = 1,4285 \frac{A}{\text{mm}^2} \\ S_3 = \frac{I_3}{A} = 2,857 \frac{A}{\text{mm}^2} \end{array} \right.$$

3

Figure 3a)

spannungsrichtige Messung:

$$R' = \frac{U}{I} = \frac{9,0 \text{ V}}{76 \text{ mA}} = 118 \Omega$$

$$R = \frac{1}{\frac{1}{R'} - \frac{1}{R_{\text{MU}}}} = \frac{1}{\frac{1}{118 \Omega} - \frac{1}{9,0 \text{ k}\Omega}} = 120 \Omega$$

(Parallelschaltung)

$$\left(\frac{1}{R'} = \frac{1}{R} + \frac{1}{R_{\text{MU}}} \right)$$

Figure 3b)

stromrichtige Messung:

$$R'' = \frac{U}{I} = \frac{10,0 \text{ V}}{80 \text{ mA}} = 125 \Omega$$

$$R = R'' - R_{\text{MI}}$$

$$R_{\text{MI}} = R'' - R = 125 \Omega - 120 \Omega = 5,00 \Omega$$

(Reihenschaltung)

$$R'' = R + R_{\text{MI}}$$

4

a) series connection

$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{\text{Kond.}} = \frac{2\pi L \varepsilon_0 \varepsilon_r}{\ln \frac{r_o}{r_i}}$$

$$C_1 = \frac{2\pi L \varepsilon_0 \varepsilon_{r1}}{\ln \frac{r_1}{r_i}}$$

$$C_1 = 24,07 \text{ nF}$$

$$C_2 = \frac{2\pi L \varepsilon_0 \varepsilon_{r2}}{\ln \frac{r_a}{r_1}}$$

$$C_2 = 8,02 \text{ nF}$$

$$C_{\text{total}} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

b)

$$Q = C \cdot U$$

$$Q = 6,015 \text{ nF} \cdot 10 \text{ kV} = 6,015 \cdot 10^{-5} \text{ As}$$

$$Q = Q_1 = Q_2$$

c)

$$\left. \begin{aligned} U_1 &= \frac{Q}{C_1} = 2,5 \text{ kV} \\ U_2 &= \frac{Q}{C_2} = 7,5 \text{ kV} \end{aligned} \right\} U_1 + U_2 = U$$

5

a) Figure 5a)

$$H_{P_1} = H_{P_2} = H_{P_3} = \frac{I}{2\pi r}$$

$$H = \frac{1000 \text{ A}}{2\pi \cdot 0,5 \text{ m}} = 318,31 \frac{\text{A}}{\text{m}}$$

b) Figure 5b)

$$P_1: \quad H_{P_1} = H_{P_1(A)} + H_{P_1(B)}$$

$$H_{P_1(A)} = \frac{I}{4\pi r} (\cos \alpha_1 - \cos \alpha_2)$$

$$= \frac{I}{4\pi r} \left(\underbrace{\cos 0^\circ}_1 - \cos 45^\circ \right)$$

$$= \frac{1000 \text{ A}}{4\pi \cdot 50 \text{ cm}} (1 - 0,707) = 0,466 \frac{\text{A}}{\text{cm}} = 46,6 \frac{\text{A}}{\text{m}}$$

$$H_{P_1(B)} = \frac{I}{4\pi r} \left(\cos 135^\circ - \underbrace{\cos 180^\circ}_{-1} \right)$$

$$= \frac{1000 \text{ A}}{4\pi \cdot 50 \text{ cm}} (-0,707 + 1) = 0,466 \frac{\text{A}}{\text{cm}} = 46,6 \frac{\text{A}}{\text{m}}$$

$$H_{P_1} = 93,2 \frac{\text{A}}{\text{m}}$$

$$P_2: \quad H_{P_2} = H_{P_2(A)} + H_{P_2(B)}$$

$$H_{P_2(A)} = 0$$

$$H_{P_2(B)} = \frac{I}{4\pi \cdot 50 \text{ cm}} \left(\underbrace{\cos 90^\circ}_0 - \underbrace{\cos 180^\circ}_{-1} \right)$$

$$H_{P_2} = \frac{1000 \text{ A}}{4\pi \cdot 50 \text{ cm}} = 1,59 \frac{\text{A}}{\text{cm}} = 159,1 \frac{\text{A}}{\text{m}}$$

$$P_3: \quad H_{P_3} = H_{P_3(B)} - H_{P_3(A)}$$

$$H_{P_3(A)} = H_{P_1(A)} = 46,6 \frac{\text{A}}{\text{m}}$$

$$H_{P_3(B)} = \frac{I}{4\pi \cdot 50 \text{ cm}} \cdot \left(\cos 45^\circ - \underbrace{\cos 180^\circ}_{-1} \right)$$

$$H_{P_3(B)} = \frac{1000 \text{ A}}{4\pi \cdot 50 \text{ cm}} (0,707 + 1) = 2,71 \frac{\text{A}}{\text{cm}} = 271,7 \frac{\text{A}}{\text{m}}$$

$$H_{P_3} = 225,1 \frac{\text{A}}{\text{m}}$$

c)

$$B = \mu_0 H$$

$$B_{P1} = \mu_0 \cdot H_{P1} = 1,257 \cdot 10^{-6} \frac{\text{Vs}}{\text{m}} \cdot 93,2 \frac{\text{A}}{\text{m}} = 1,17 \cdot 10^{-4} \text{ T}$$