

NEISSE - ELEKTRO 2015

Name:

1	2	3	4	5	Σ

Tasks for the finale test
90 min; with formula sheet (English edition)

1

Two conductors of Aluminium and Copper with the same cross section of $A = 2,5 \text{ mm}^2$ are connected in series and a current of $I = 12 \text{ A}$ is flowing through both.

- Calculate the amounts of the current density S and the electric field strength E in both conductors for the following specific electrical resistances:
Copper $\rho = 0,017 \cdot 10^{-6} \text{ } \Omega\text{m}$
Aluminium $\rho = 0,027 \cdot 10^{-6} \text{ } \Omega\text{m}$
- Which cross section would be necessary for the aluminium conductor to have the same electric field strength E in both conductors?
- How long must be the aluminium conductor, to have the same resistance R than a copper conductor of a length of 10 m for both with the same cross section ($A = 2,5 \text{ mm}^2$)?
- Calculate the amount of this resistance R !

2

An Edison electric lamp with the following parameters $P_N = 60 \text{ W}$ and $U_N = 230 \text{ V}$ has an Wolfram heating wire ($\rho_{20} = 0,055 \text{ } \Omega \text{ mm}^2 / \text{m}$) with a length of $l = 60 \text{ cm}$ and a diameter of $d = 0,03 \text{ mm}$.

- Calculate the temperature of the heating wire in service ($\alpha = 0,0041 / \text{K}$)
- Calculate the current I and the electrical power P during switch-on at a temperature of $\vartheta = 20 \text{ } ^\circ\text{C}$

(Help: Calculation of the resistance at service temperature: $P_N = U_N I_N$ and $R_B = U_N / I_N$)

3

Given is the electrical circuit according to figure 1

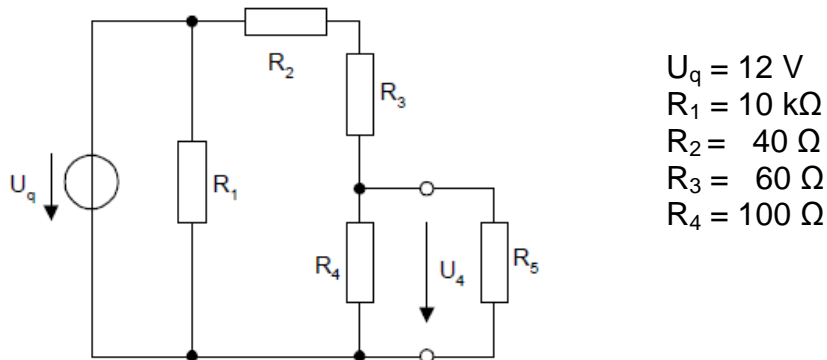


Figure 1

- Calculate the voltage U_4 without the resistance R_5 in this circuit!
- Which amount must have the resistance R_5 that the voltage U_4 is just 10 % of the voltage U_q ?
- Calculate for this case of b) the currents I_1 up to I_5 and the total current I_G of the voltage source!

4

Given is the series connection of 3 capacitors according to figure 2

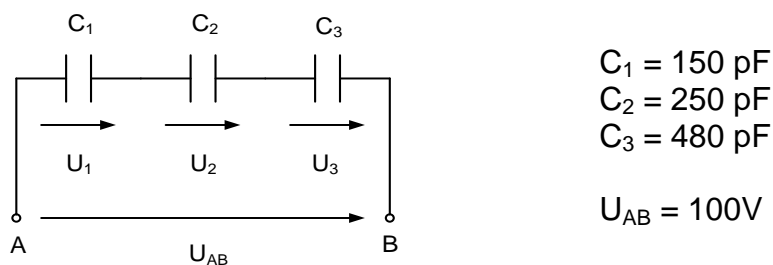


Figure 2

- Calculate the total Capacitance C_{AB} the total Charge Q_{AB} and the voltages U_1 , U_2 and U_3 !
- To which amounts the total Capacitance C_{AB} , the total Charge Q_{AB} and the voltages U_1 , U_2 and U_3 will change in case of a breakdown of the capacitor C_3

5

In an infinite long conductor is the current flow of a direct current $I = 100 \text{ A}$

- Calculate the amount of the magnetic field strength H and of the magnetic flux density (magnetic induction) B in a distance of $r = 10 \text{ cm}$!
- Calculate the length l of the conductor to have in point P (see figure 3) 90% of the magnetic field strength H compared to the infinite long conductor!

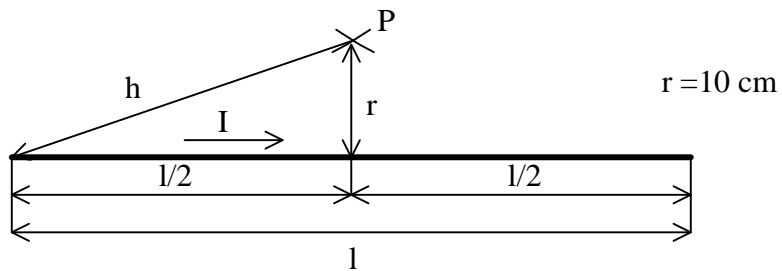


Figure 3