

NEISSE - ELEKTRO 2000


Name:

1	2	3	4	5	S

Tasks for the finale
90min ; with formulary (english edition)


1

Calculate $U_o = f(\Delta R)$!

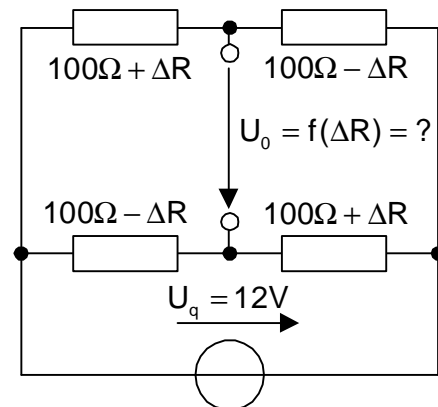

2

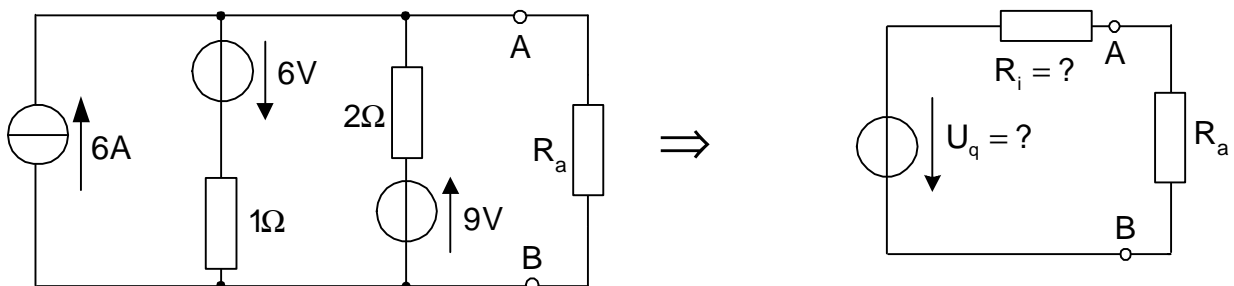
The left circuit is given. Transform it in the right circuit and calculate U_q and R_i !



3


A filament lamp $P_N = 60\text{W}$; $U_N = 230\text{V}$ is connected in series with a coil (resistance $R_{sp} = 100\Omega$, inductivity L) and supplied by ac voltage
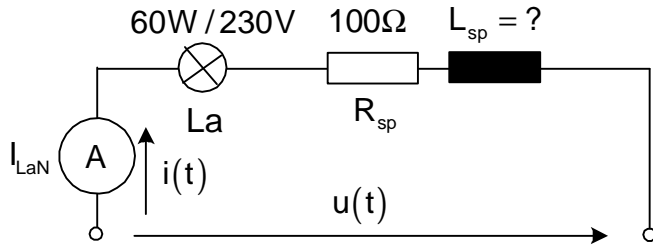
$$u(t) = \sqrt{2} \cdot 400\text{V} \cdot \cos(2\pi \cdot 50\text{Hz} \cdot t + 45^\circ)$$



Calculate the necessary value of the inductivity L of the coil, for operation the filament lamp with its nominal values!

4

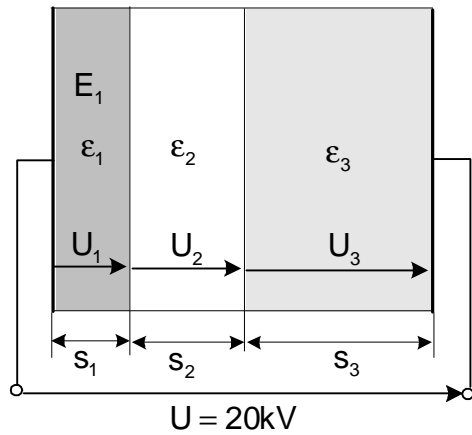

The following plate capacitor is given

$$s_1 = 1,5\text{cm} \quad \epsilon_{r1} = 6,5$$


$$s_2 = 2,0\text{cm} \quad \epsilon_{r2} = 1$$

$$s_3 = 2,5\text{cm} \quad \epsilon_{r3} = 4$$

$$\epsilon_0 = 8,85 \cdot 10^{-12} \text{As/Vm}$$

- Calculate the electrical strength of the field E_1 in the dielectric 1!
- Calculate the voltages U_1 , U_2 , U_3 !

5

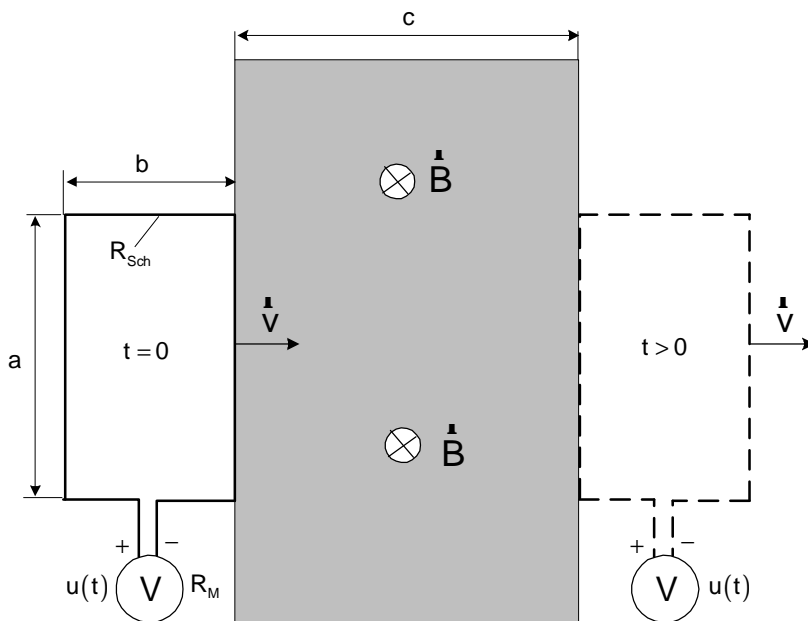

The wire-loop ($a = 50\text{mm}$, $b = 30\text{mm}$) is moved with a speed of $v = 0,2\text{m/s}$ through the homogeneous magnetic field ($B = 1\text{T}$, $c = 60\text{mm}$).

Calculate the variation in time of the voltage $u(t)$, displayed on the voltmeter!
(R_M ? R_{Sch})

